

EXPERIMENT 4: Single phase rectifiers

Name -

Mehul Kavdia (2018A8PS0860P)

Yash Raj Agarwal (2018A8PS0782P)

Pranamyia Jain (2018A8PS0769P)

Jash Shah (2018A8PS0507P)

Sec No. - 4

Group No. - 10

Date - 17/03/21

Objective - To study load voltage and current waveforms of single-phase full wave rectifiers under:

- a) Controlled rectification
- b) Uncontrolled rectification
- c) Midpoint rectification


for firing angles $\alpha = 45, 60$ and 90 deg respectively.

Software tool: MATLAB Simulink, Simscape toolbox (power GUI)

Components used:


Detailed thyristor; Diode; AC source; Step-down transformer; Pulse generator; Resistor, inductor and constant dc-side voltages as load; Voltage and current sensors; Display; Scope

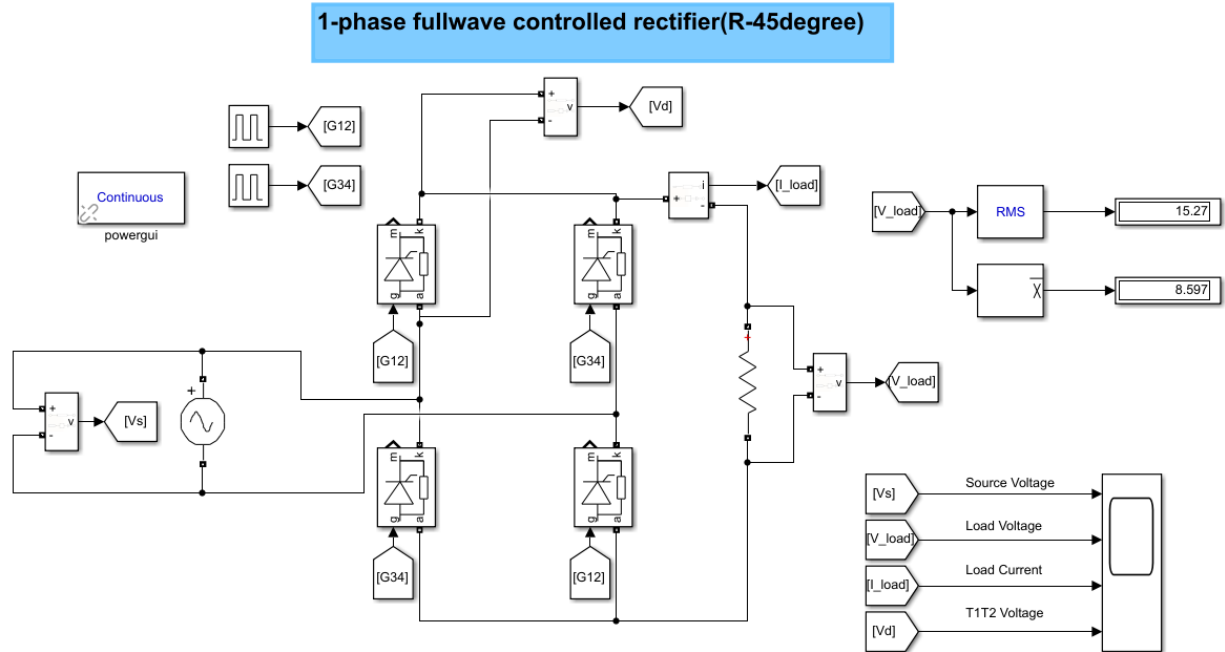1. Single phase full wave controlled rectifier - R load(100 ohms)




1(a) $\alpha = 45^\circ$

$V_{rms} = 15.27V$, $V_{avg} = 8.597V$

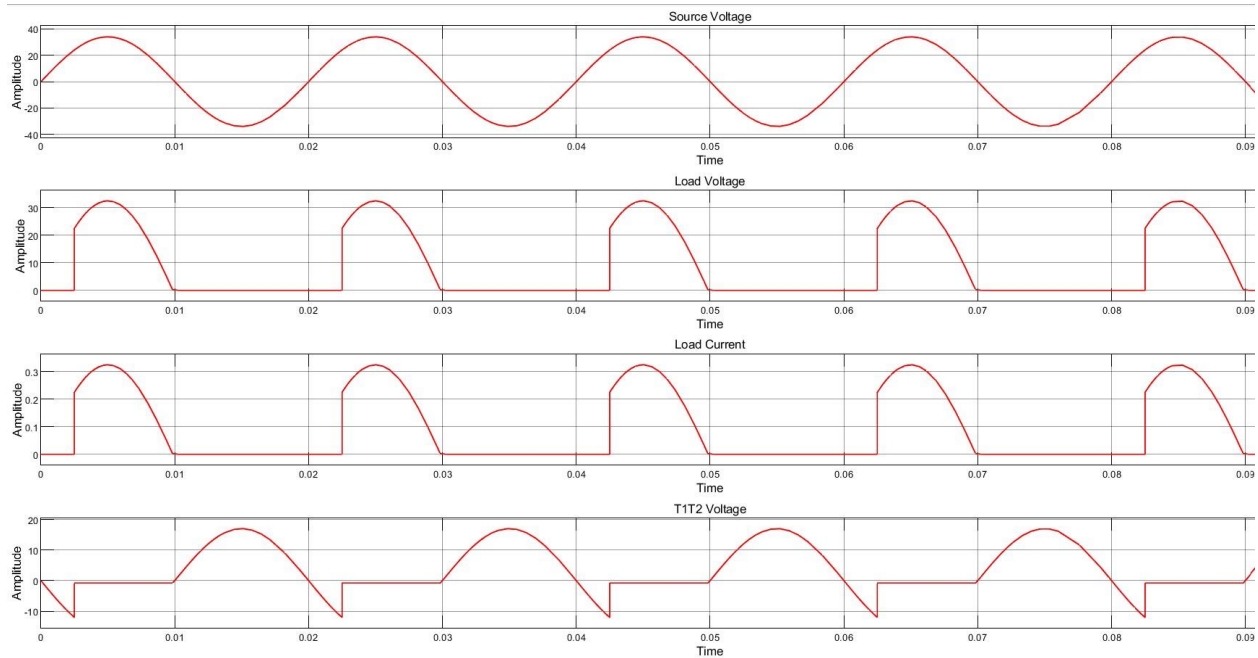


1(b) $\alpha = 60^\circ$

$V_{rms} = 14.45V$, $V_{avg} = 7.6V$

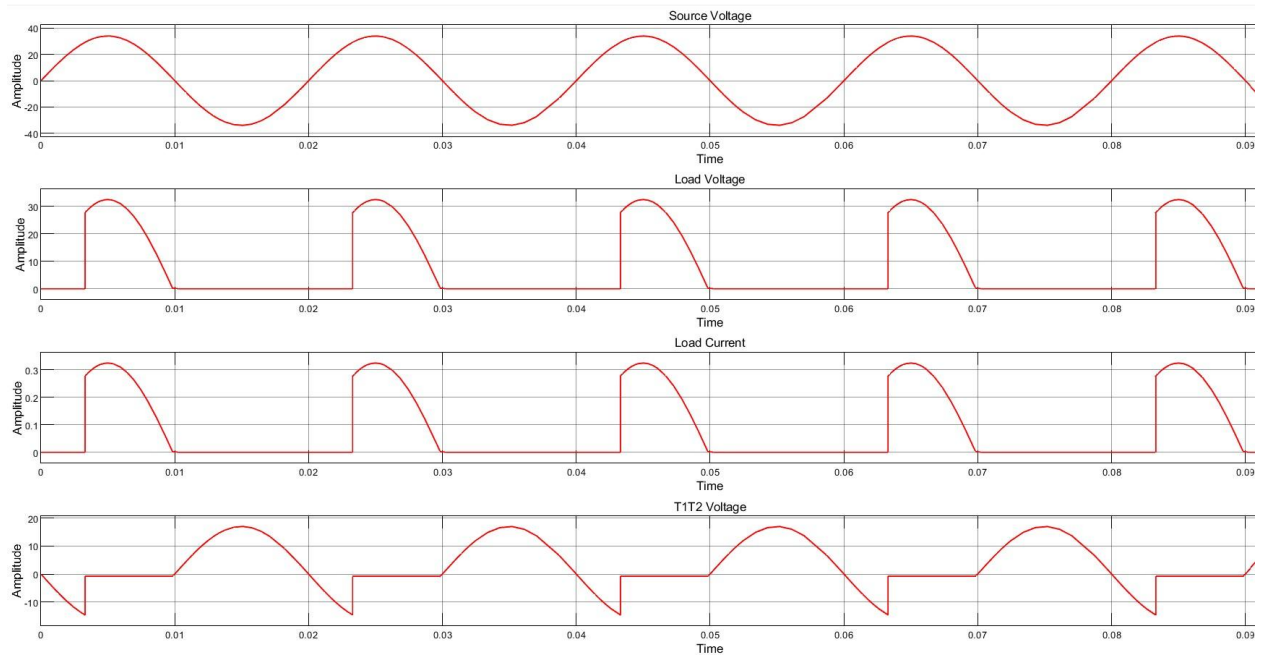


1(c) $\alpha = 90^\circ$

$V_{rms} = 11.34V$, $V_{avg} = 5V$

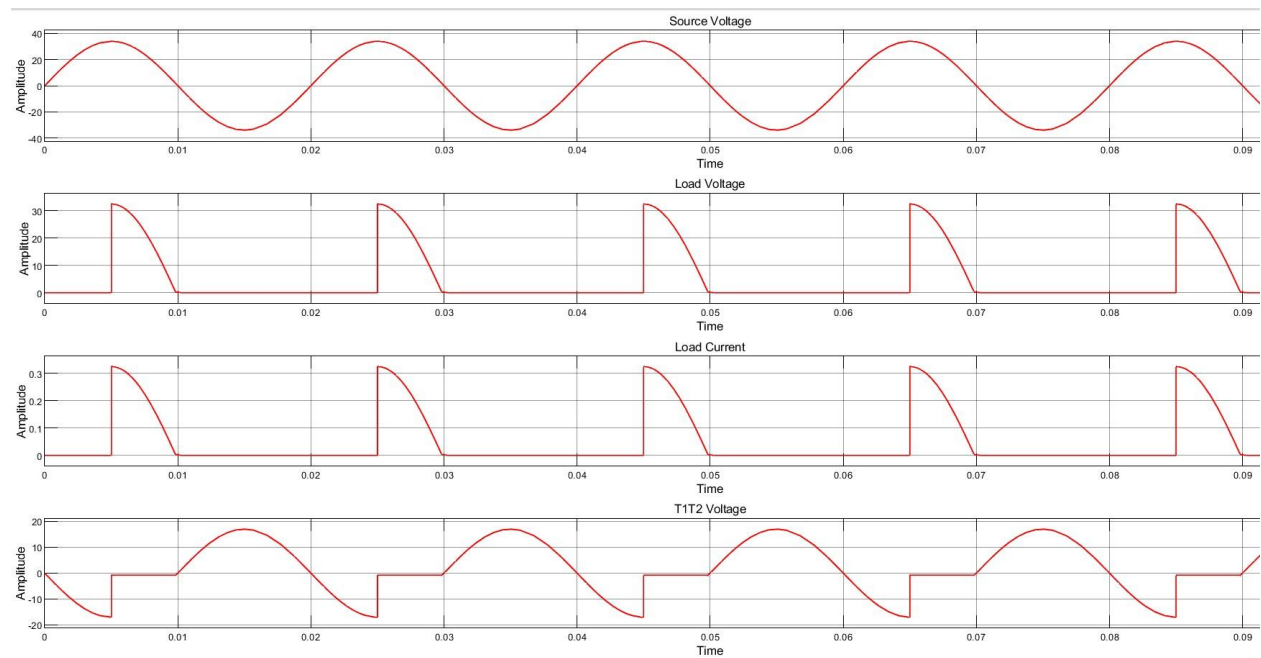


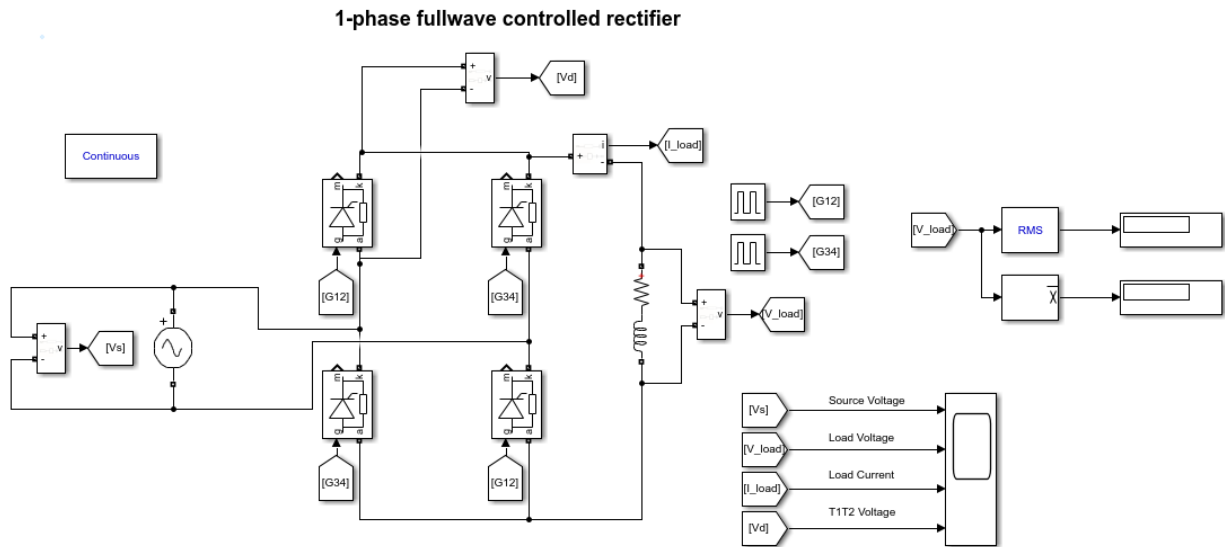2. Single phase full wave controlled rectifier RL load(100 ohms, 150uH)




2(a) $\alpha = 45^\circ$

$V_{rms} = 15.26V$, $V_{avg} = 8.596V$

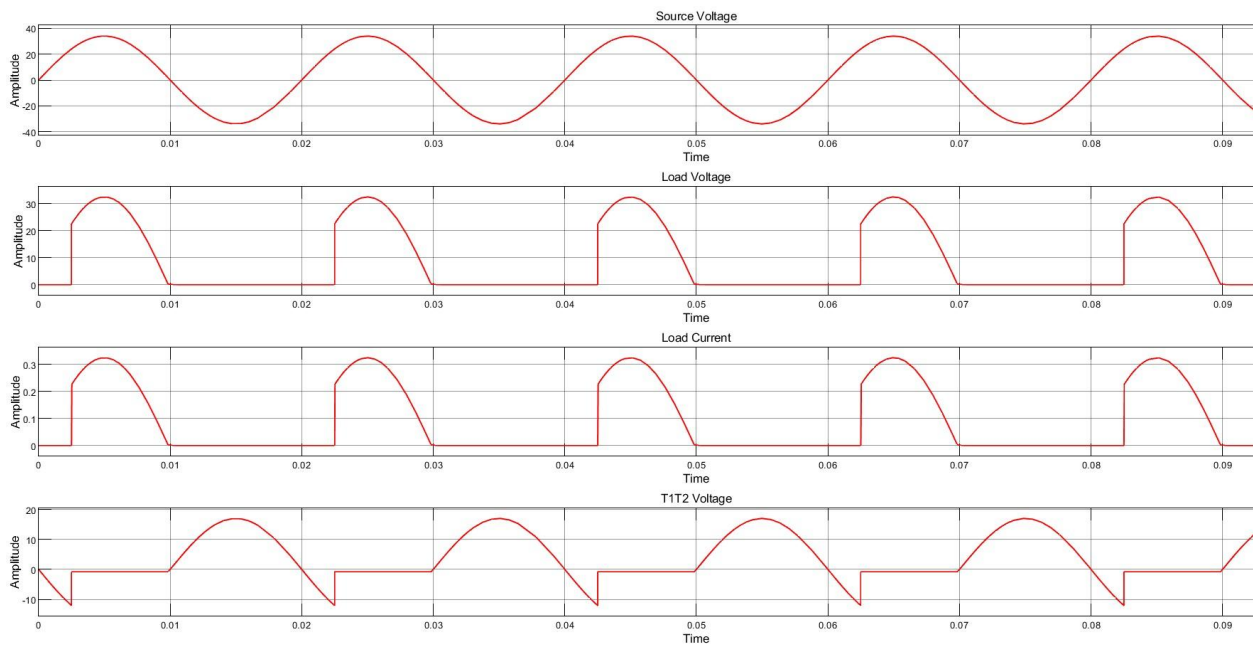


2(b) $\alpha = 60^\circ$

$V_{rms} = 14.43V$, $V_{avg} = 7.6V$

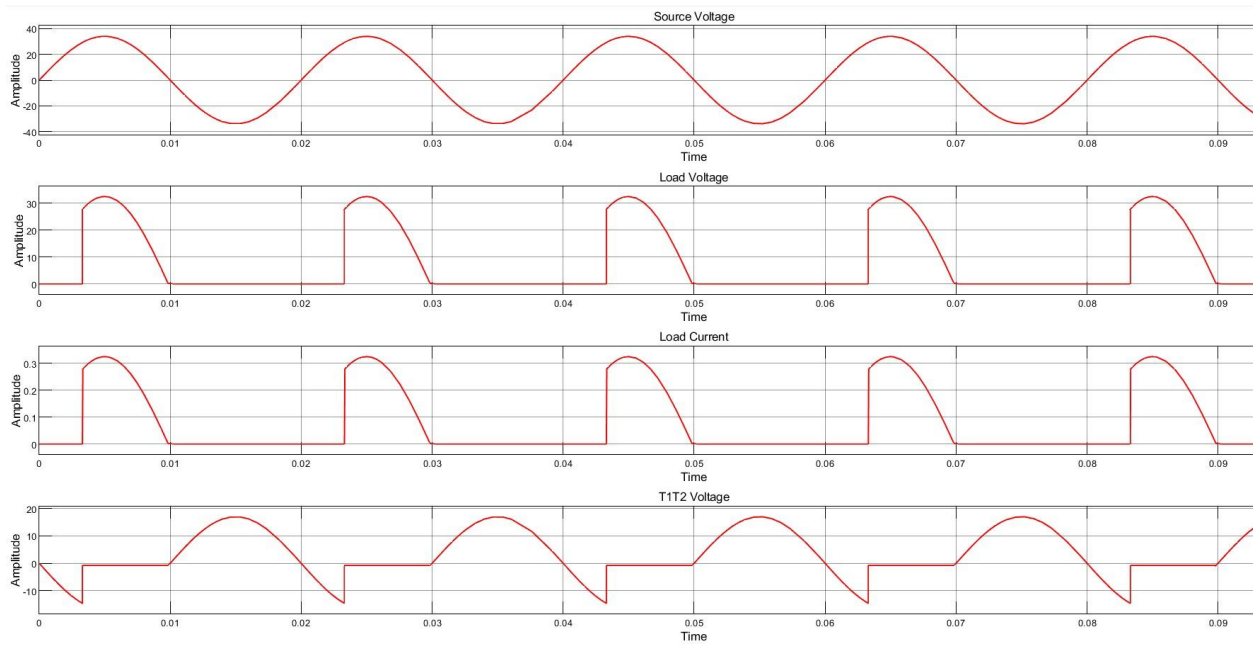


2(c) $\alpha = 90^\circ$

$V_{rms} = 11.33V$, $V_{avg} = 5V$

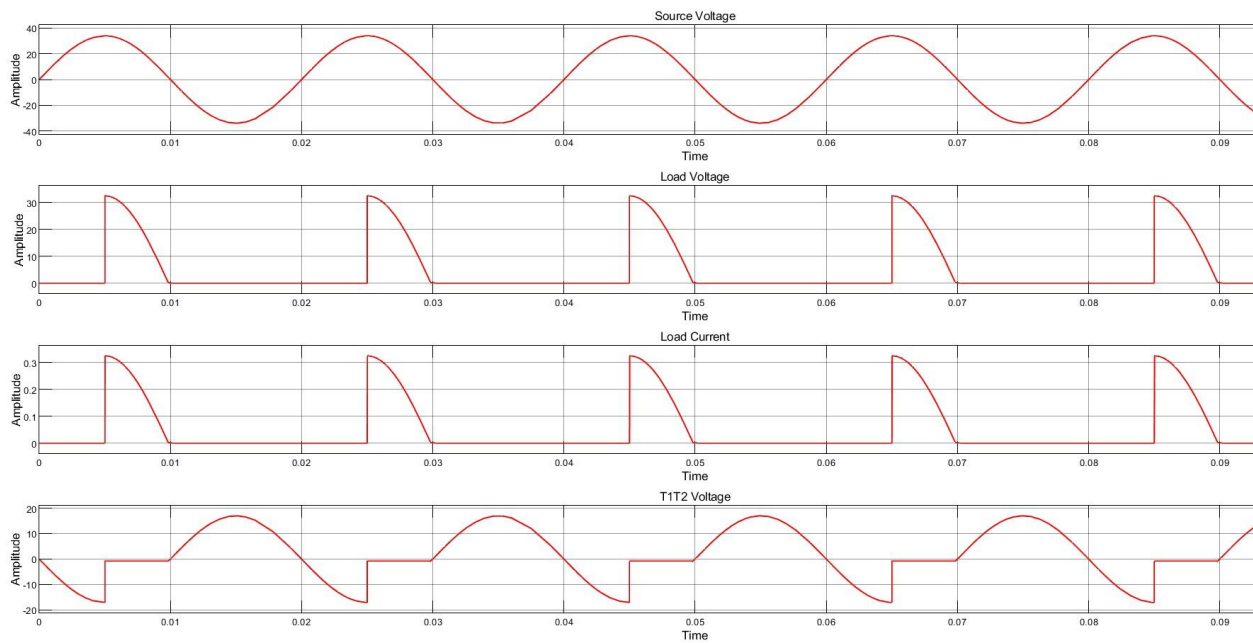


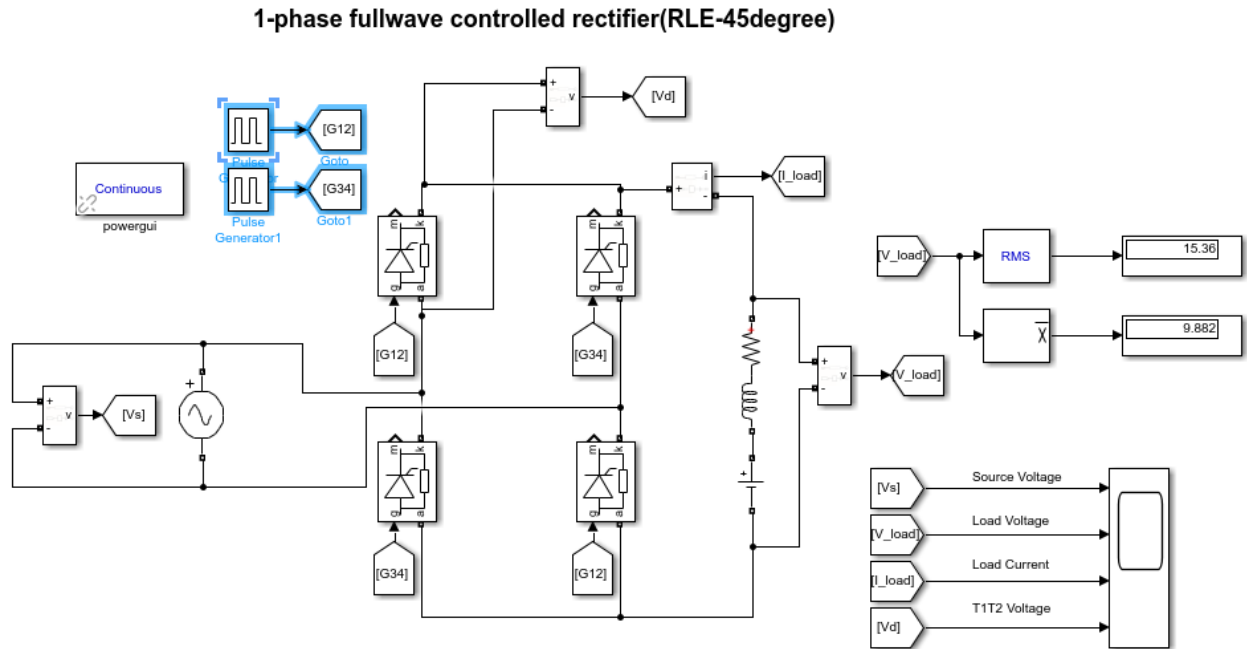3. Single phase full wave controlled rectifier RLE load(100 ohms, 150uH, 2V)




3(a) $\alpha = 45^\circ$

$V_{rms} = 15.36V$, $V_{avg} = 9.882V$

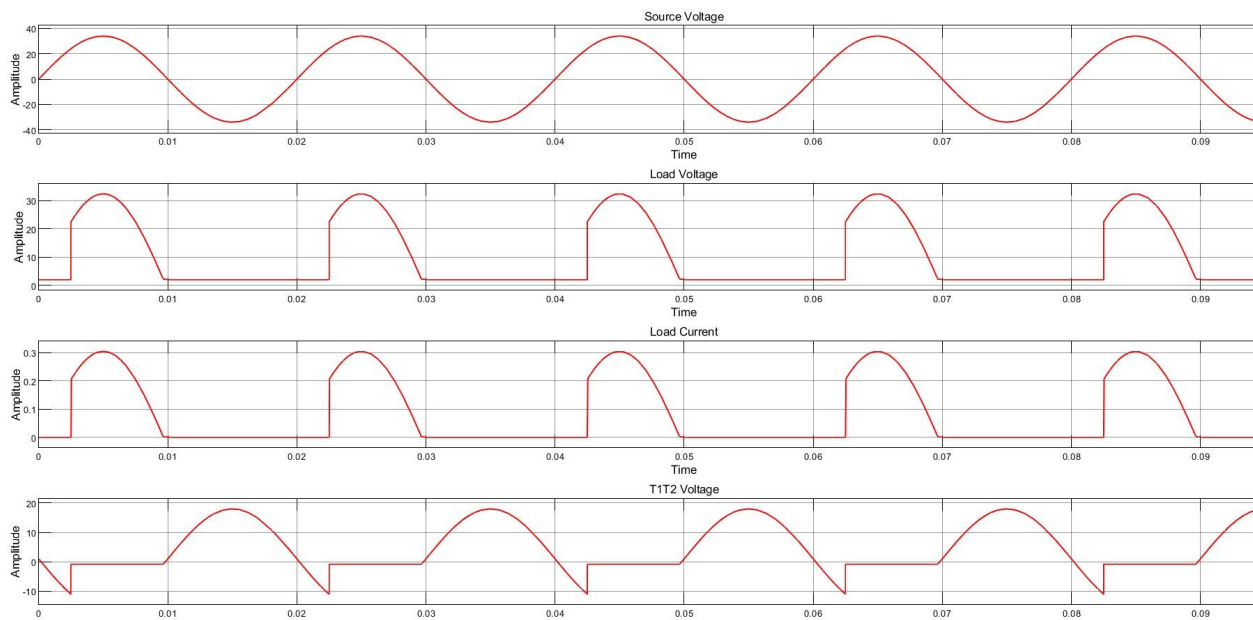


3(b) $\alpha = 60^\circ$

$V_{rms} = 14.53V$, $V_{avg} = 8.95V$

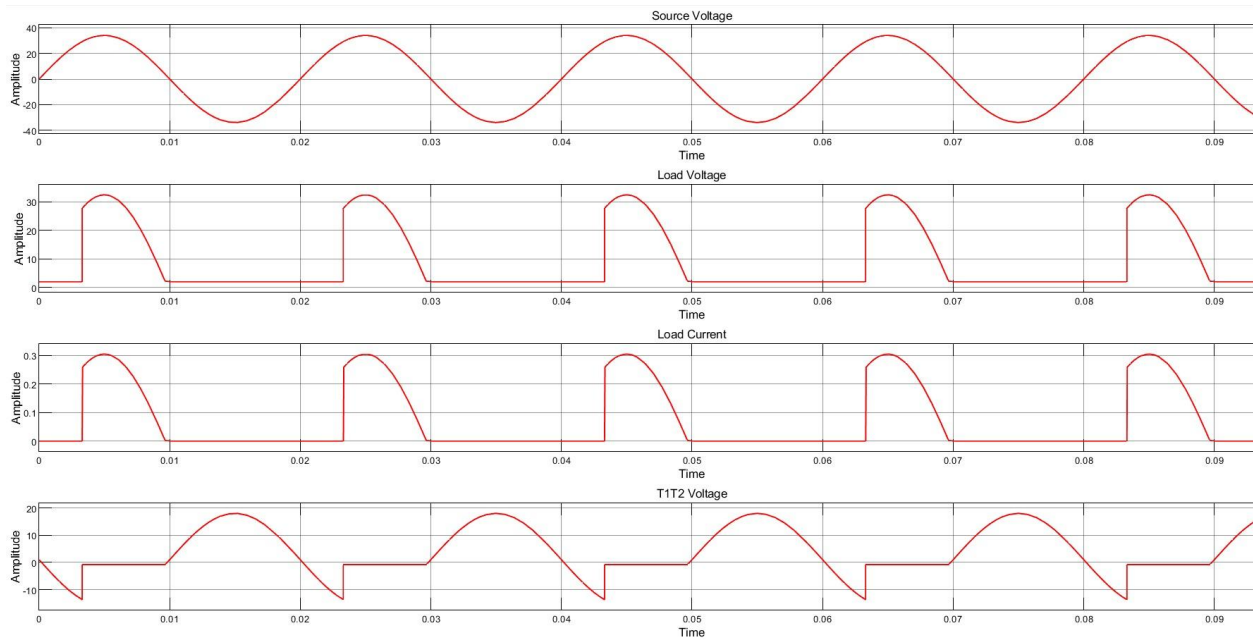

3(c) $\alpha = 90^\circ$

$V_{rms} = 11.45V$, $V_{avg} = 6.54V$

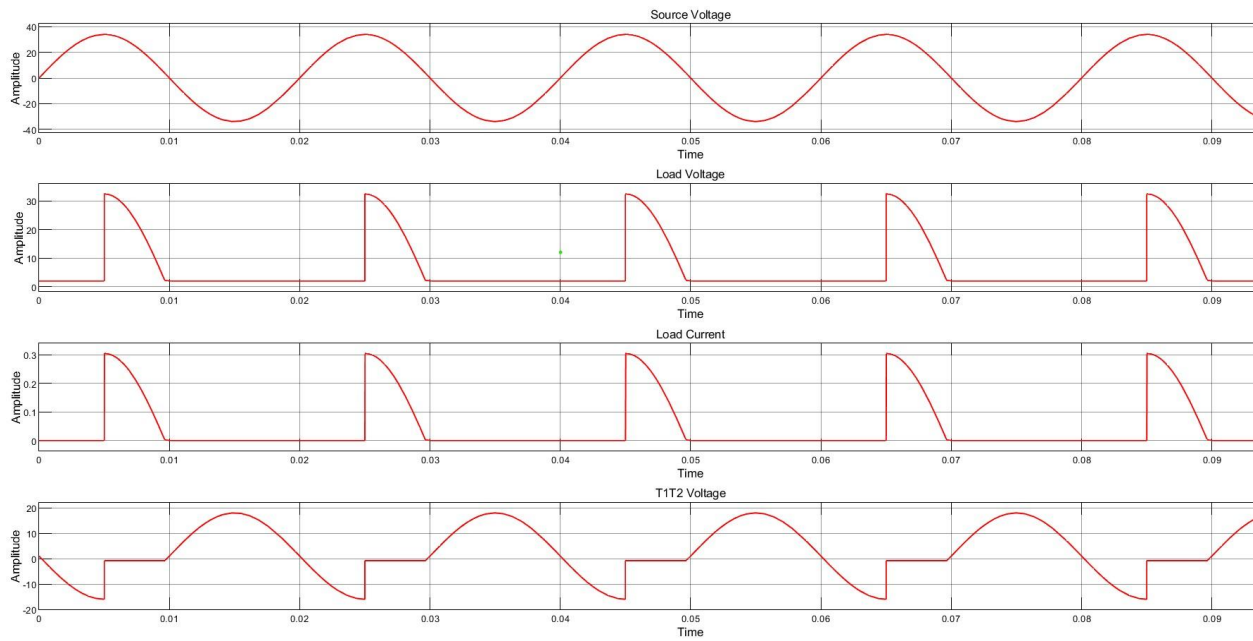


Controlled Full wave rectifier table:

Components	α	Output Voltage (Vd)	
		Practically	Theoretically
R			
	45°	21.59	18.475
	60°	20.4	16.234
	90°	15.99	10.82
RL			
	45°	21.60	18.475
	60 °	20.41	16.234
	90°	15.99	10.82
RLE			
	45°	21.61	18.475


	60°	20.44	16.234
	90°	16.06	10.82

4. Single phase full wave uncontrolled rectifier R load(100 ohms)


1-phase fullwave uncontrolled rectifier

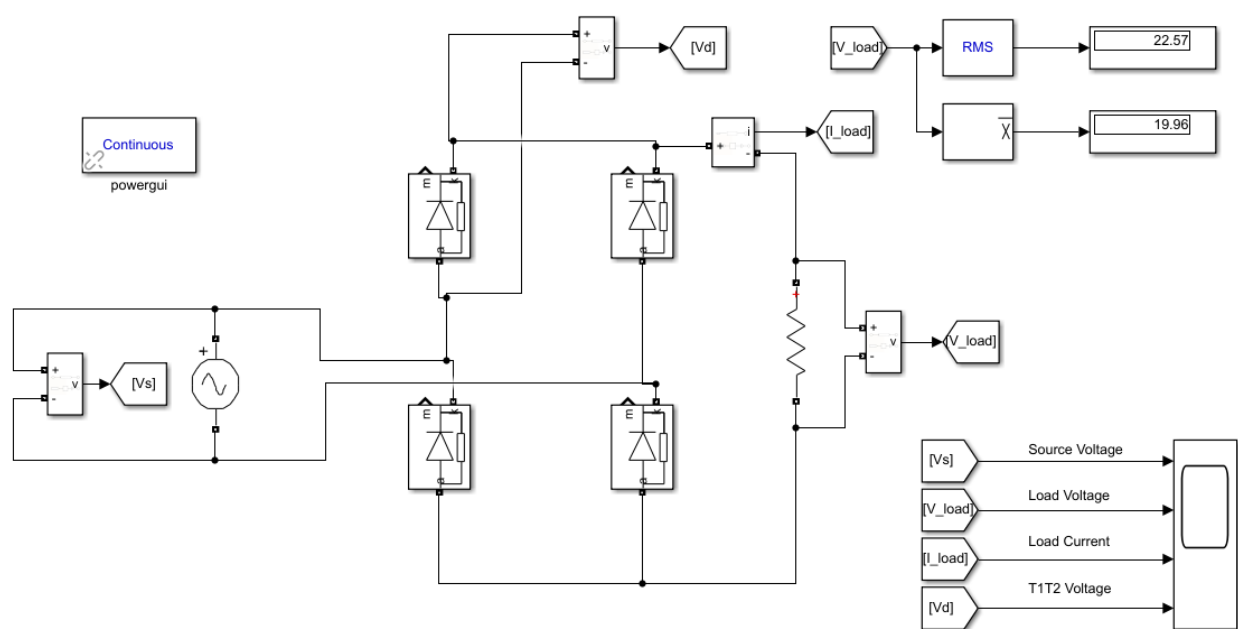


$$V_{rms} = 22.57V, V_{avg} = 19.96V$$

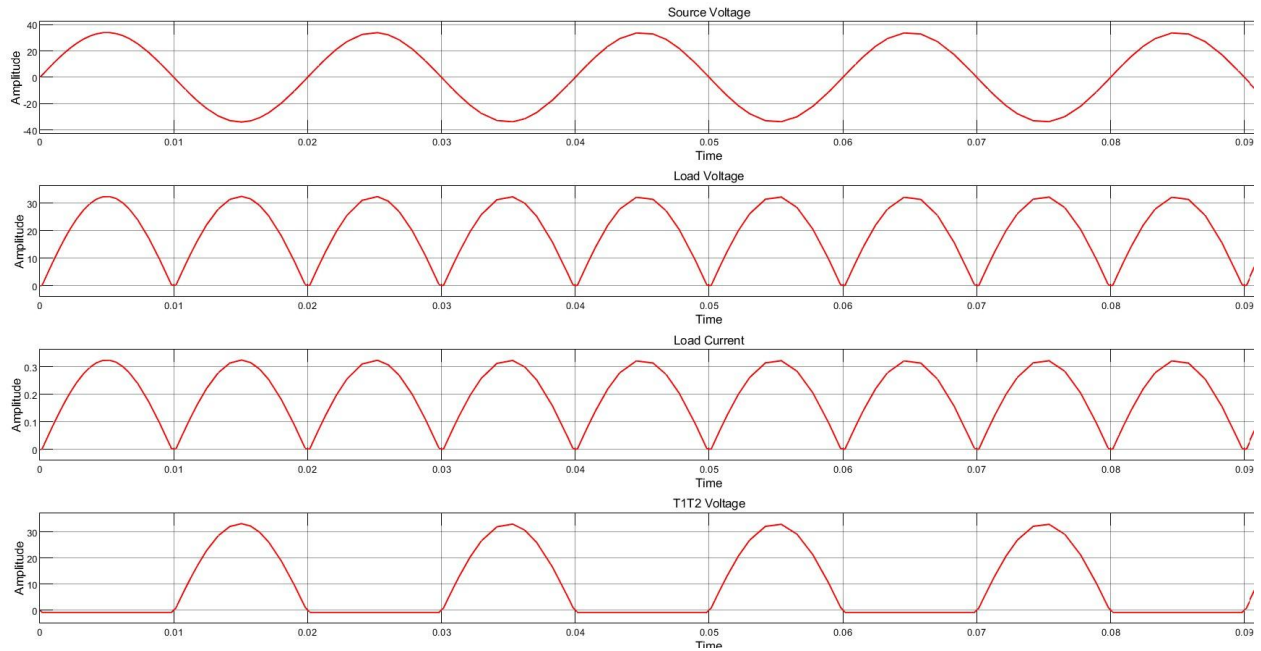

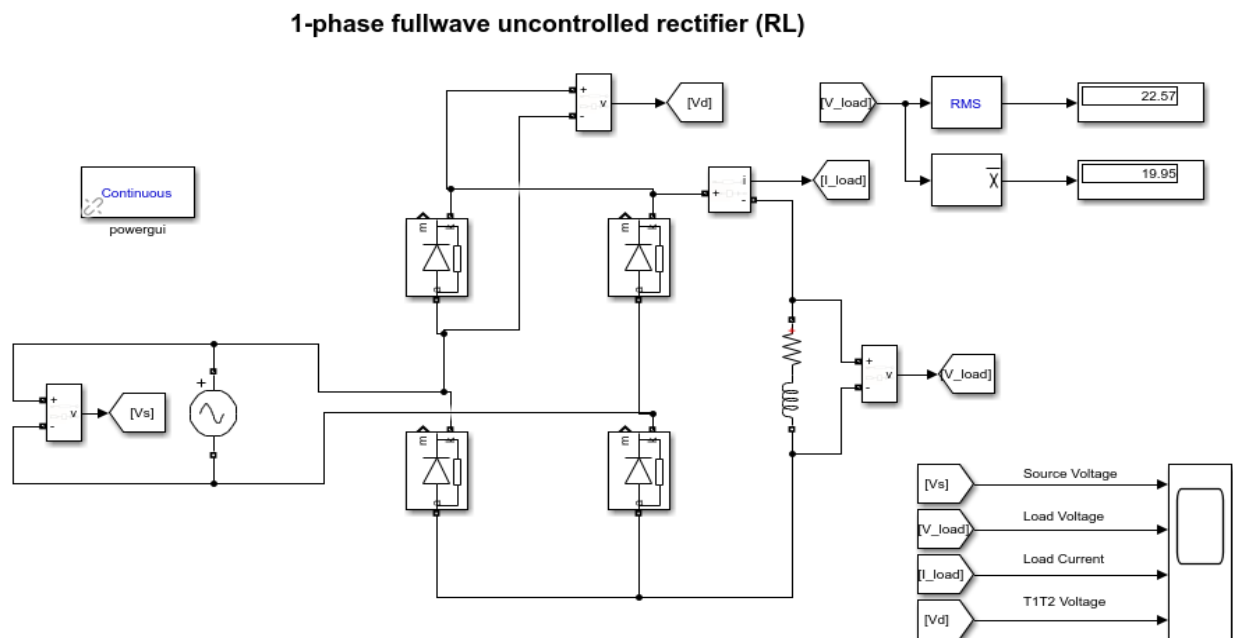5. Single phase full wave uncontrolled rectifier RL load(100 ohms, 150uH)




$$V_{rms} = 22.57V, V_{avg} = 19.95V$$

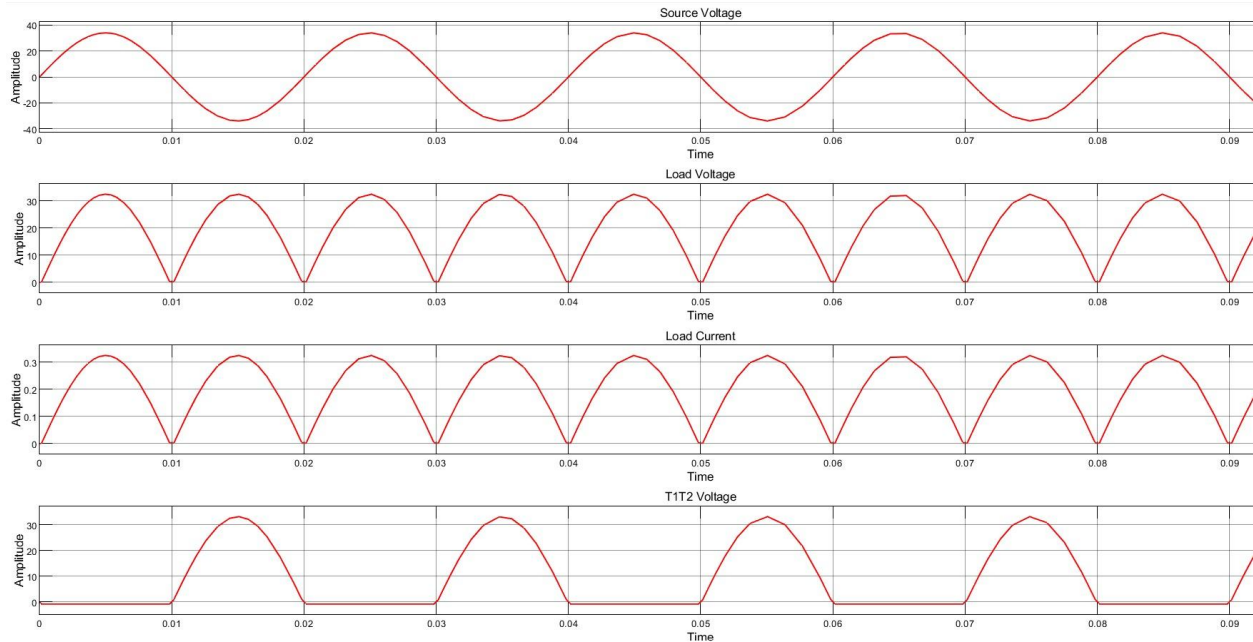


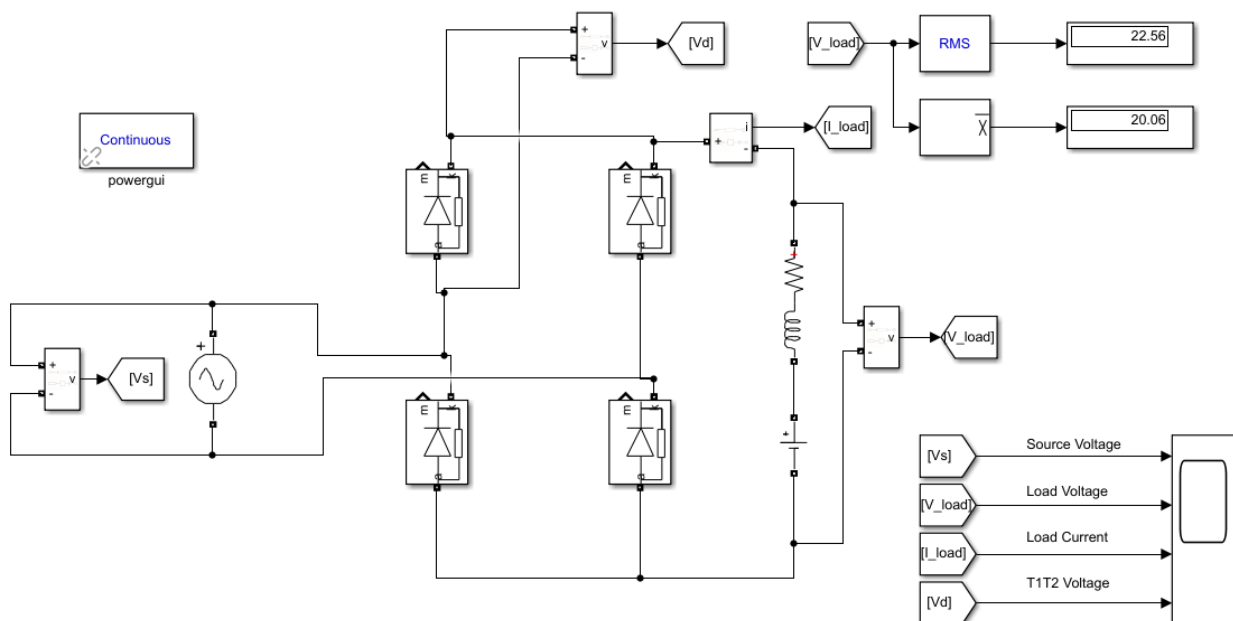6. Single phase full wave uncontrolled rectifier RLE load(100 ohms, 150uH, 2V)

1-phase fullwave uncontrolled rectifier(RLE)



$$V_{rms} = 22.56V, V_{avg} = 20.06V$$

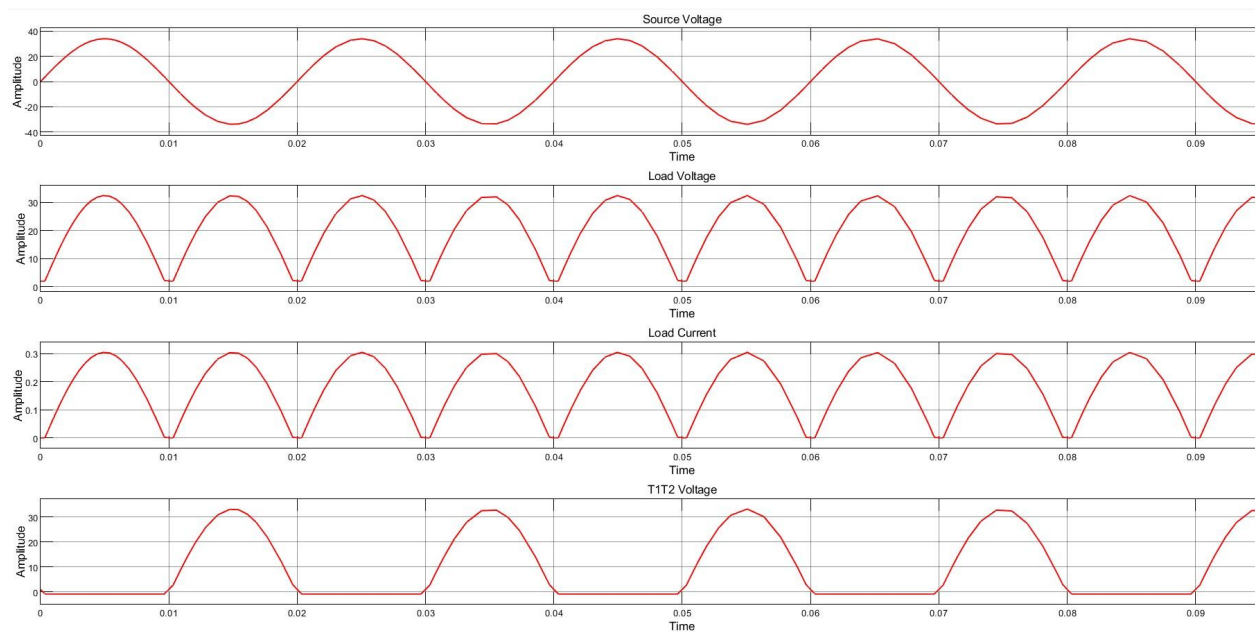


Uncontrolled Full wave rectifier table:

Components	Output Voltage (Vd)	
	Practical y	Theoretical ly
R	22.56	21.645

RL	22.57	21.645
RLE	22.57	21.645

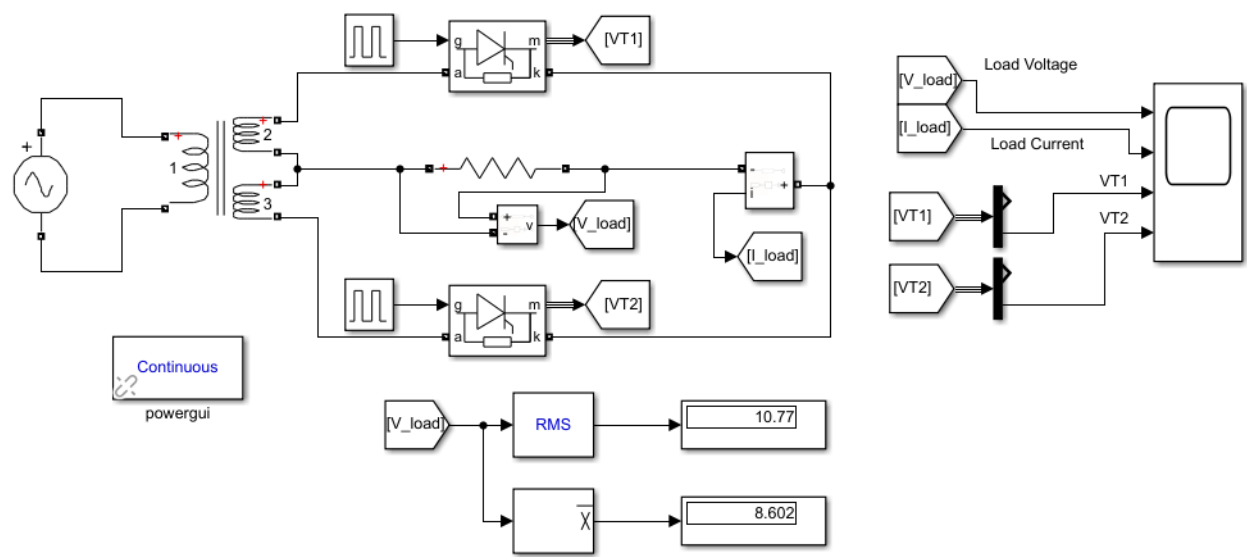
7. Single phase mid point full wave rectifier R load(100 ohms)

1-phase mid point fullwave rectifier(R-45degree)




7(a) $\alpha = 45^\circ$

$V_{rms} = 10.77V$, $V_{avg} = 8.6V$

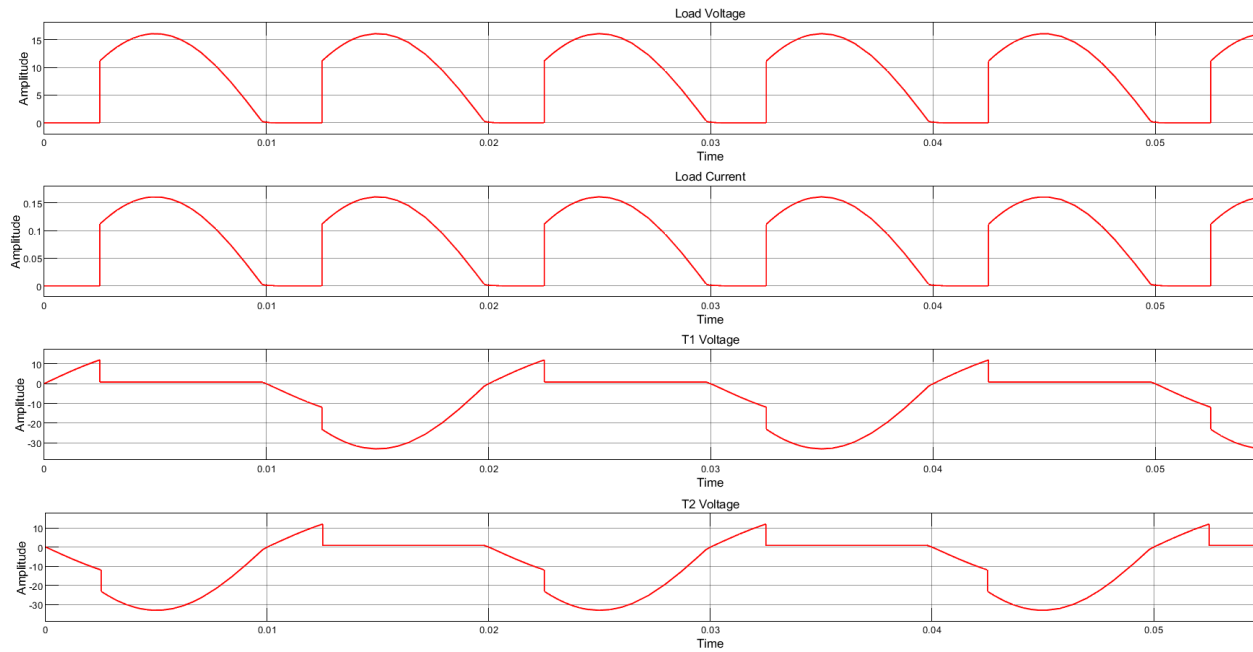


7(b) $\alpha = 60^\circ$

$V_{rms} = 10.17V$, $V_{avg} = 7.59V$

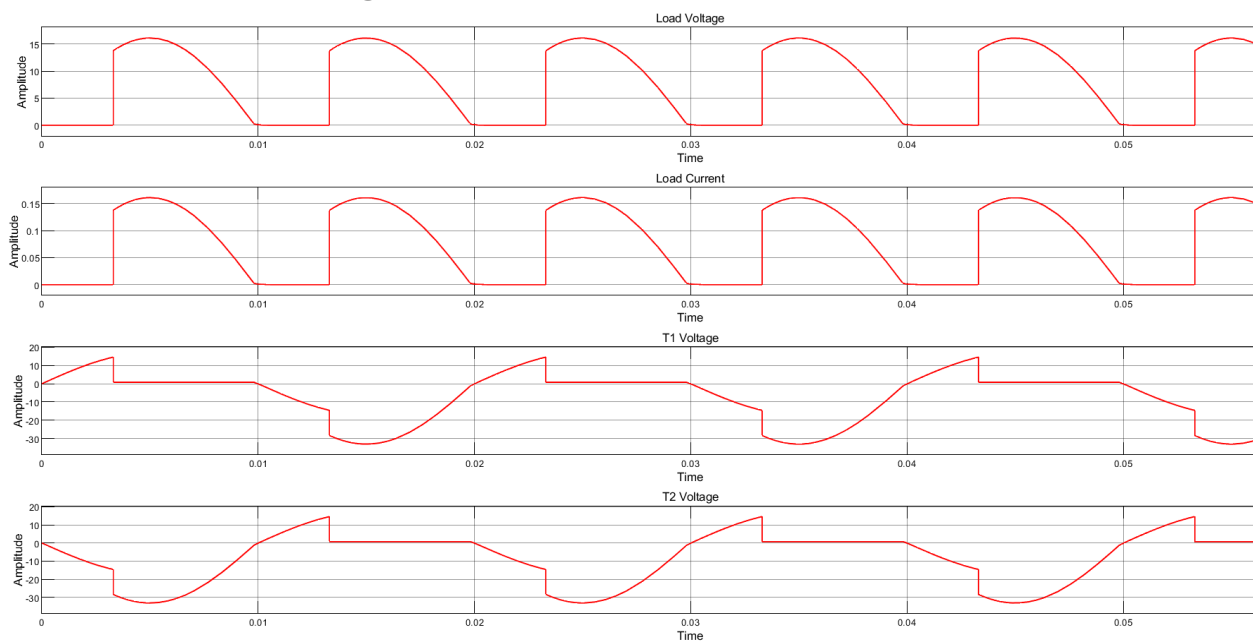


7(c) $\alpha = 90^\circ$

$V_{rms} = 7.96V$, $V_{avg} = 4.96V$

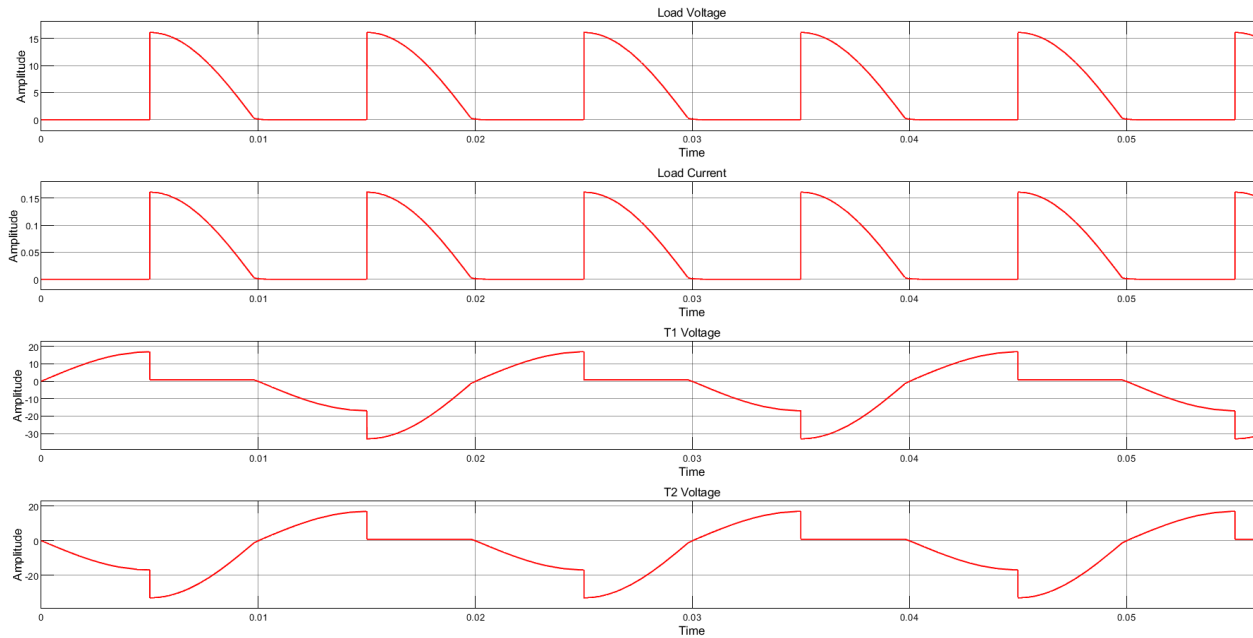

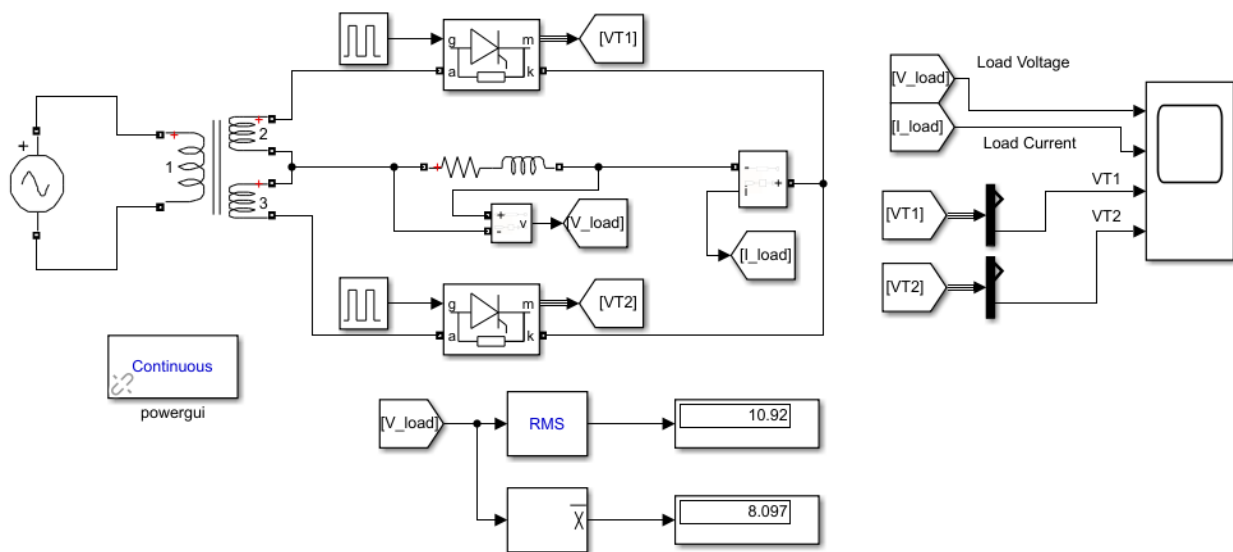
8. Single phase mid point full wave rectifier RL load(100 ohms, 150mH)

1-phase mid point fullwave rectifier($R=45\text{degree}$)




8(a) $\alpha = 45^\circ$

$V_{rms} = 10.92V$, $V_{avg} = 8.097V$

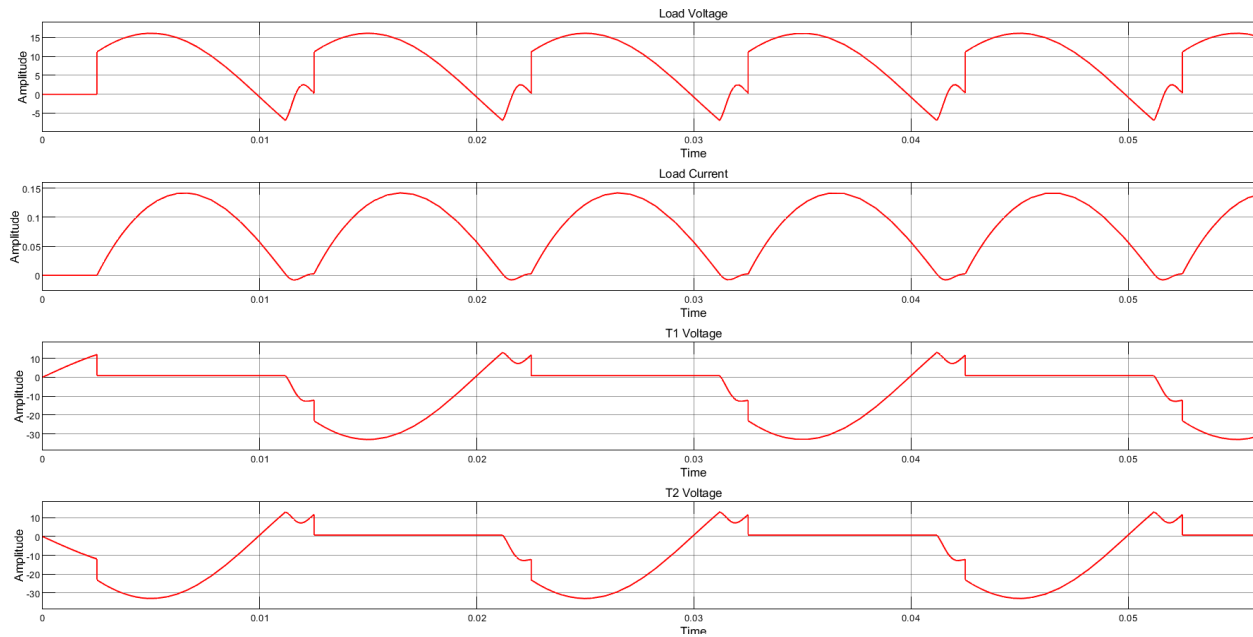


8(b) $\alpha = 60^\circ$

$V_{rms} = 10.35V$, $V_{avg} = 7.035V$

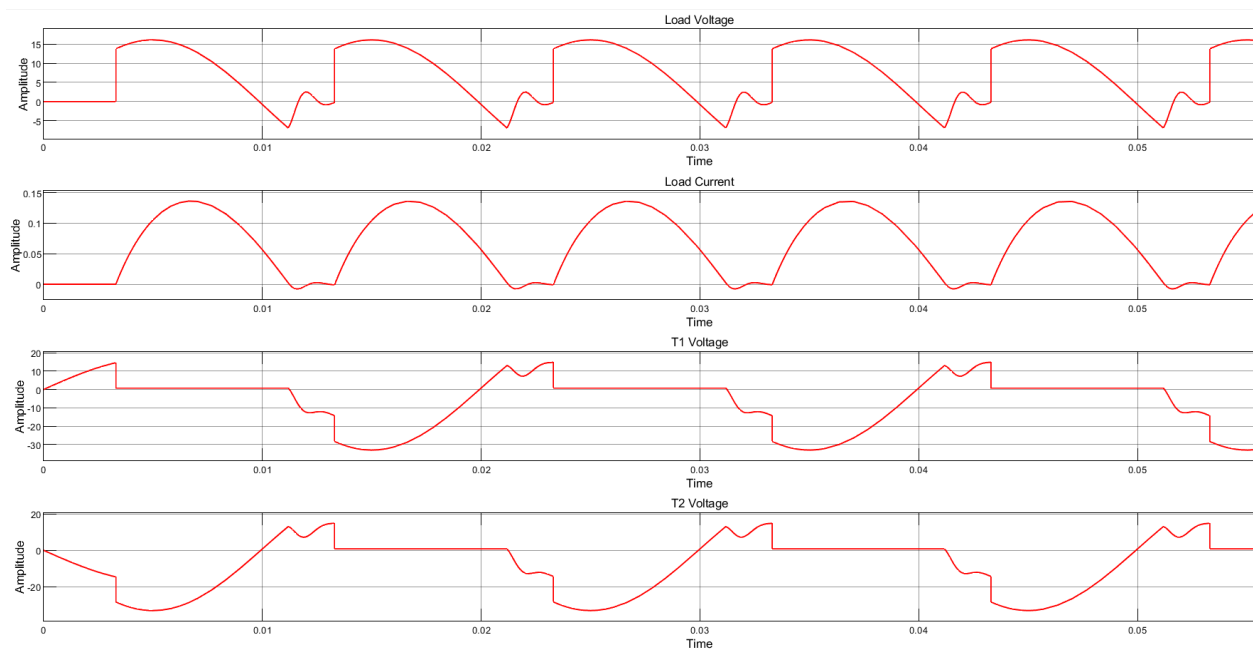

8(c) $\alpha = 90^\circ$

$V_{rms} = 8.149V$, $V_{avg} = 4.48V$

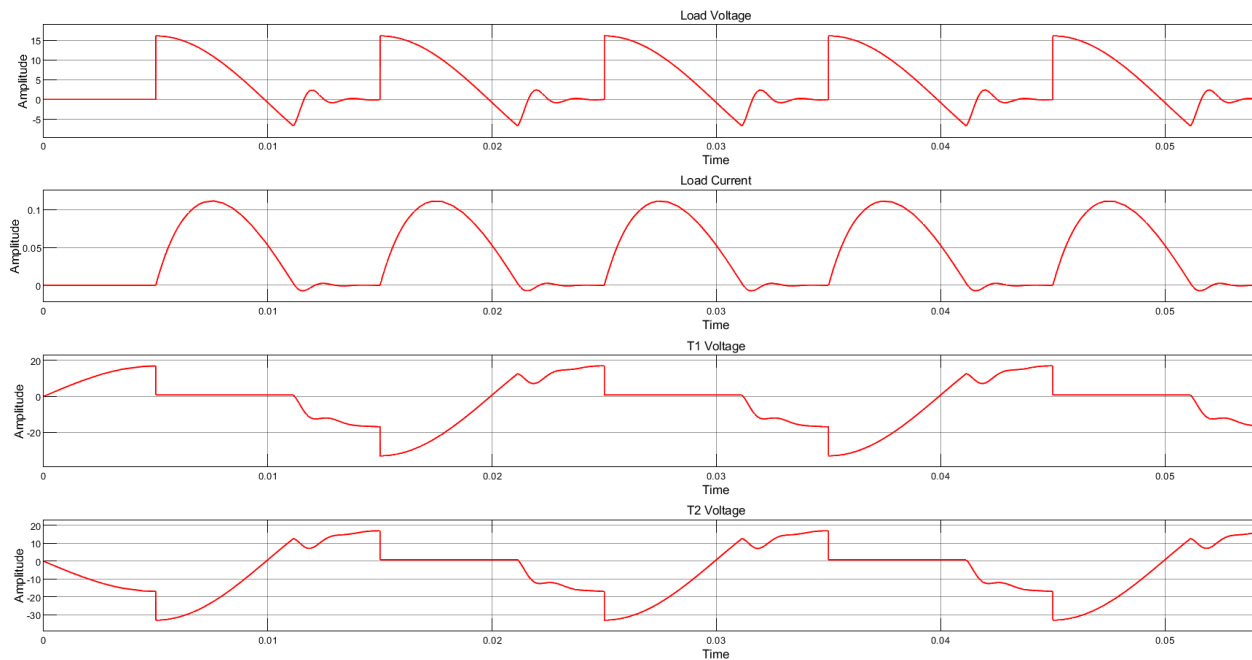

Calculation Table

	Uncont rolled	Contr olled	Mid-Point
Average output voltage	21.645V	15.31V	146.4225V

RMS output voltage	24.042V	24.04V	162.634V
Peak load current	0.2404A	0.24A	1.626A
Average load current	0.21645 A	34V	0.146A
Peak inverter voltage	34V	0.15A	230V
Power delivered to load	7.357W	5.77W	23.744W
Ripple voltage	10.462V	10.46V	70.771V
Ripple factor	0.482	0.482	0.482
Form factor	1.11	1.57	1.11